

PHYSICS

Ans 1:- (a) Electrical resistance - ohm

(b) Resistivity - ohm-meter

Ans 2:- One ohm is the resistance of a conductor such that when a potential difference of 1 volt is applied to its ends and a current of 1 ampere flows through it.


Ans 3:- Resistance

- Resistance is the property of a conductor to resist the flow of charges through it.

Resistivity

- Resistivity is the electrical resistance per unit length and per unit of cross-sectional area.

Ans 4:- (a) Rheostat

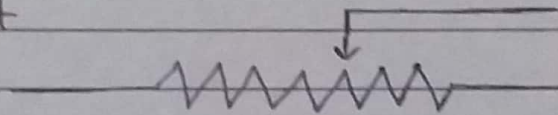

(b) Closed key



Ans 5:- The rate at which the work is being done in an electrical circuit is called electrical power.

The SI unit is Watts (W).

Ans 6:- Current (I) = 0.2 A

Time (t) = 5 hours = (3600 × 5) sec.

$$\text{Current} = \frac{\text{Charge}}{\text{Time}}$$

$$I = \frac{Q}{t}$$

$$Q = I \times t$$

$$= 0.2 \times 3600 \times 5$$

$$Q = 3600 \text{ coulomb.}$$

Ans 7:-

$$V_0 = 12 \text{ V}$$

$$I = 2.5 \text{ mA} = 2.5 \times 10^{-3} \times 10 = 25 \times 10^{-4}$$

$$R = ?$$

$$R = \frac{V}{I}$$

$$R = \frac{12}{25 \times 10^{-4}}$$

$$R = \frac{12 \times 10^4}{25}$$

$$R = \frac{12 \times \overset{2000}{10000}}{\underset{25}{5}}$$

$$R = 4800 \text{ ohms.}$$

Ans 8:- (1) In Series

$$\text{Total resistance in series} = R_1 + R_2$$

$$= 2 + 2$$

$$= 4 \text{ ohm}$$

$$\text{Potential difference (V)} = 12 \text{ V}$$

$$\text{Current (I)} = \frac{V}{R}$$

$$= \frac{12}{4} = 3 \text{ Ampere}$$

$$\text{Power} = V \times I$$

$$= 12 \times 3$$

$$= 36 \text{ Watts.}$$

(2) In parallel

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_a}$$

(where R_a is the total resistance)

$$\frac{1}{2} + \frac{1}{2} = \frac{1}{R_a}$$

$$\frac{2}{2} = \frac{1}{R_a}$$

$$R_a = 10 \Omega$$

$$\text{Voltage (V)} = 12 \text{ V}$$

$$\text{Current (I)} = \frac{V}{R}$$

$$= 12 \text{ Ampere.}$$

$$\text{Power} = V \times I$$

$$= 12 \times 12 = 144 \text{ W}$$

$$\text{Ratio} = 1:4$$

Ans 9) - Power $\propto \frac{1}{\text{Resistance}}$

\therefore Lesser the power more is resistance

For first lamp:-

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} \Rightarrow \frac{1210}{48400} \times 10^6$$

$$R = 1210 \Omega$$

For lamp 1:-

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{220^2}{40} = 1210 \Omega$$

$$R = 1210 \Omega$$

∴ Electric lamp having 40W; 220V has a higher resistance.

∴ The lamp having less resistance will glow brighter, i.e., lamp 2.

Ques 10:- (a) A month has approximately 30 days.

In according to data present in question,

The electricity consumption of one day is:-

$$(i) \text{ Refrigerator} = (400 \times 10) = 4000 \text{ Wh}$$

$$(ii) 2 \text{ fans} = (2 \times 80 \times 12) = 1920 \text{ Wh}$$

$$(iii) 6 \text{ Tubes} = (6 \times 18 \times 6) = 648 \text{ Wh}$$

$$\text{Total} = (4000 + 1920 + 648) = 6568 \text{ Wh} = 6.568 \text{ kWh}$$

$$= 6.6 \text{ units}$$

$$\text{Electricity consumption of one month} = 6.6 \times 30$$

$$= 198 \text{ units}$$

$$\text{Total cost} = 198 \times 3 = ₹ 594$$

$$(b) \text{ Resistance } (R) = 20 \Omega$$

$$\text{Current } (I) = 5 \text{ A}$$

$$\text{Time } (t) = 30 \text{ sec.}$$

$$\text{Heat} = I^2 R t$$

$$H = 5^2 \times 20 \times 30$$

$$H = 25 \times 600$$

$$H = 15000 \text{ J}$$

$$H = 1.5 \times 10^4 \text{ J}$$

Q.11:- Ammeter is always connected in series with a resistive element ~~due~~ to because due to low resistance act like short circuit there are chances of ammeter to get damaged.

Q.12:- Copper and Aluminium wires are used as connecting wires because they have low resistivity and high conductivity.

Q.13:- Tungsten metal is used as filament of electric lamps because tungsten can sustain high temperatures and it has high melting points and also has high resistivity.

Q.14:- When a electric charge ^(Q) moves against a potential difference (V) then amount of work done is:

$$W = V \times Q \quad \text{--- (1)} \quad \left(\because V = \frac{W}{Q} \right)$$

$$\text{Using } V = I \times R \quad \text{--- (2)}$$

~~Substituting eq (1) & (2)~~

$$W = I \times t \quad \text{--- (3)} \quad \left(\because I = \frac{Q}{t} \right)$$

Put (2) and (3) in (1)

$$W = (I \times R) (I \times t)$$

$$W = I^2 R t$$

$$W = H \quad (\because \text{Heat produced})$$

$$H = I^2 R t$$

This reaction is called Joules law of heating.

Q-15 (a) Derivation of Series Resistance

Let R_1, R_2, R_3 be three resistors combined in series with a potential difference (V) and current passing through it be (I)

$$V_1 = I \times R_1$$

$$V_2 = I \times R_2$$

$$V_3 = I \times R_3$$

$$(V_1 + V_2 + V_3) = I (R_1 + R_2 + R_3)$$

Replacing V_1, V_2, V_3 by (V)

$$\frac{V}{I} = R_1 + R_2 + R_3$$

$$V = I R_e$$

Derivation of Parallel Resistance

Let R_1, R_2, R_3 be three resistances connected in parallel with a potential difference (V)

$$I_1 = V/R_1$$

$$I_2 = V/R_2$$

$$I_3 = V/R_3$$

$$I_1 + I_2 + I_3 = V/R_1 + V/R_2 + V/R_3$$

Replacing $I_1 + I_2 + I_3$ by I

$$I = V (1/R_1 + 1/R_2 + 1/R_3)$$

$$V/R_e = V (1/R_1 + 1/R_2 + 1/R_3) \quad (\because I = V/R_e)$$

$$\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Hence Proved

Royal